
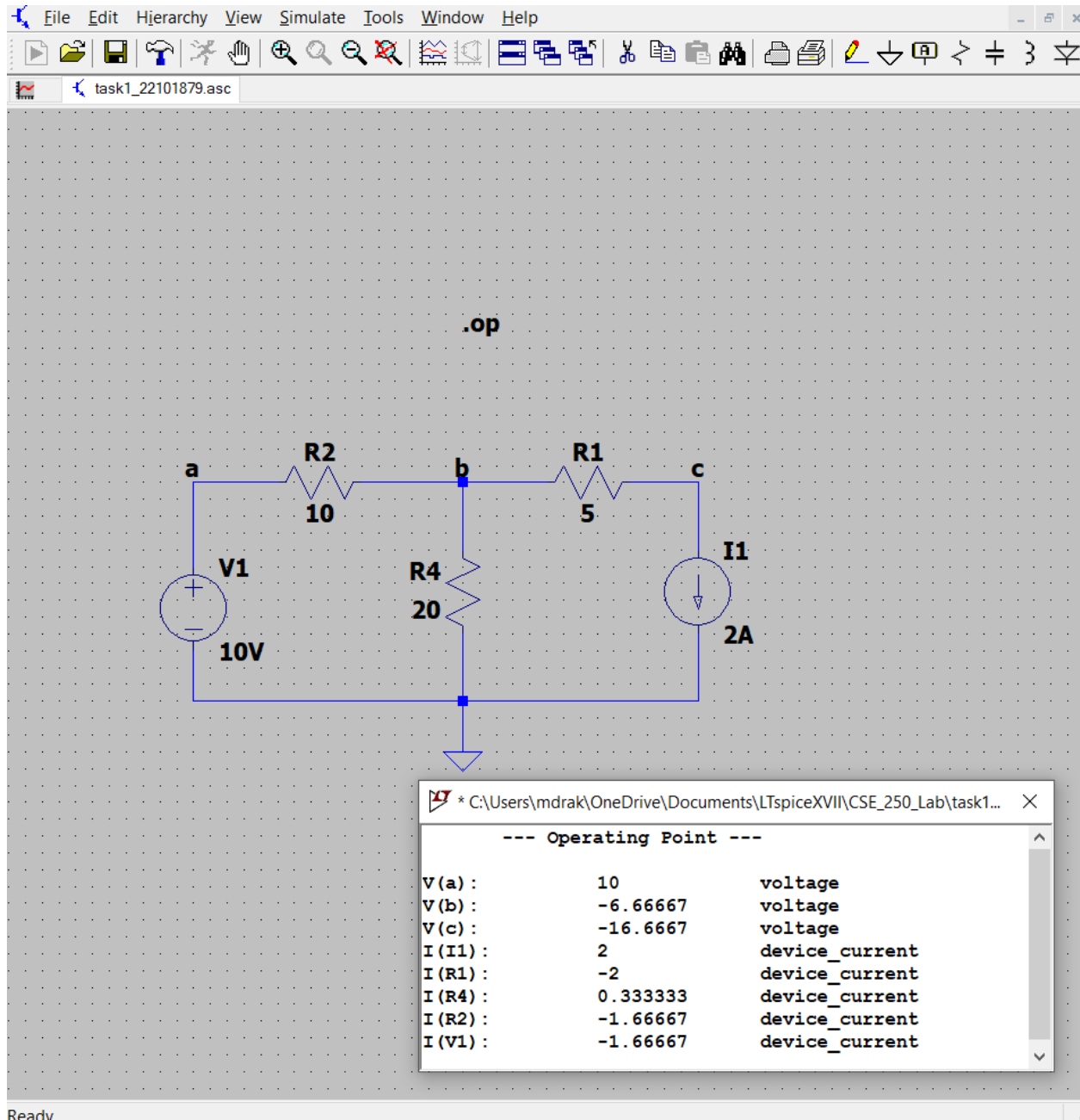


Name: MD Rakib Hossain Ontu  
Id:22101879  
Sec: 16  
Group: 04


### task1

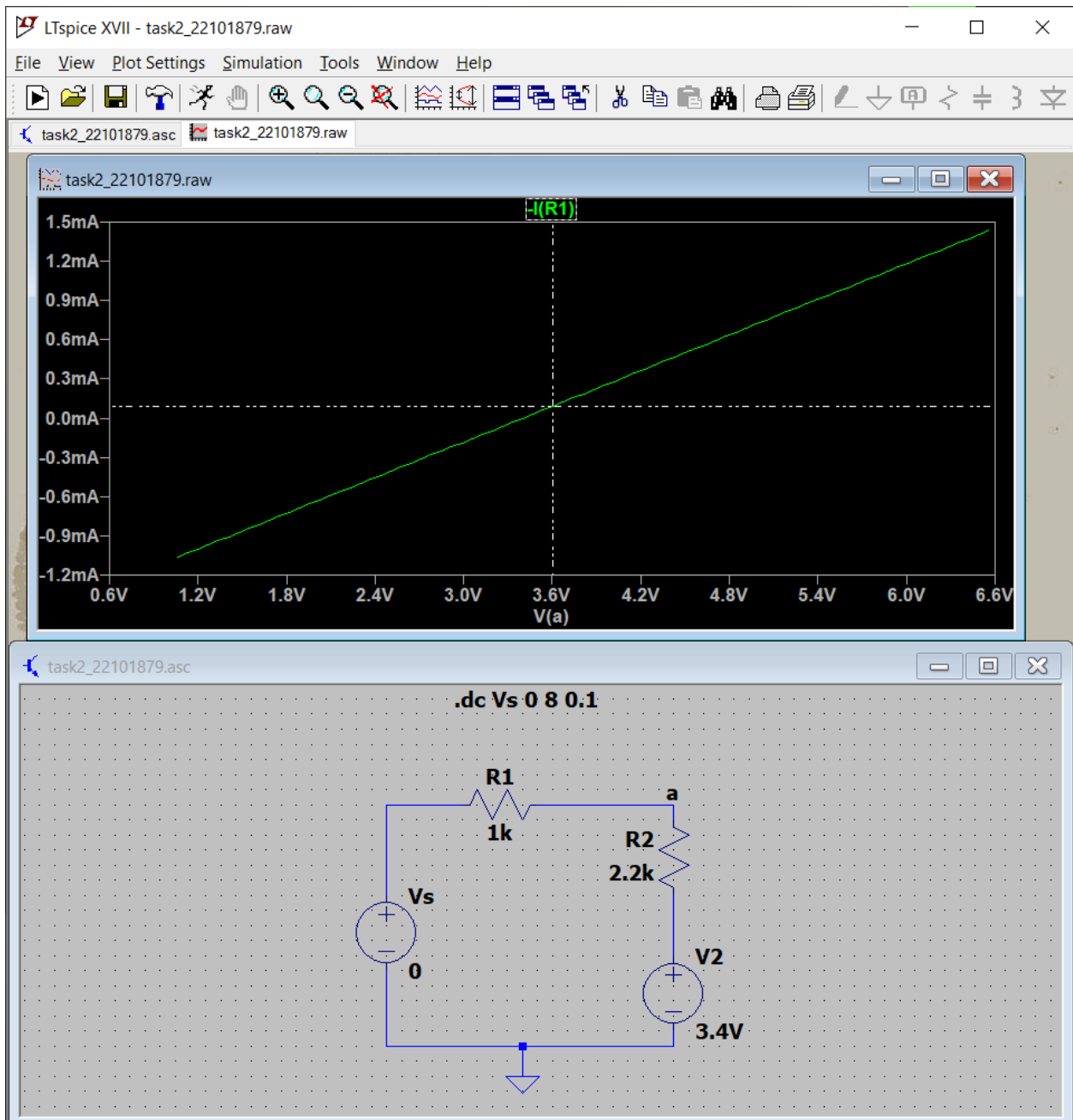


## Task2




### Task3.1

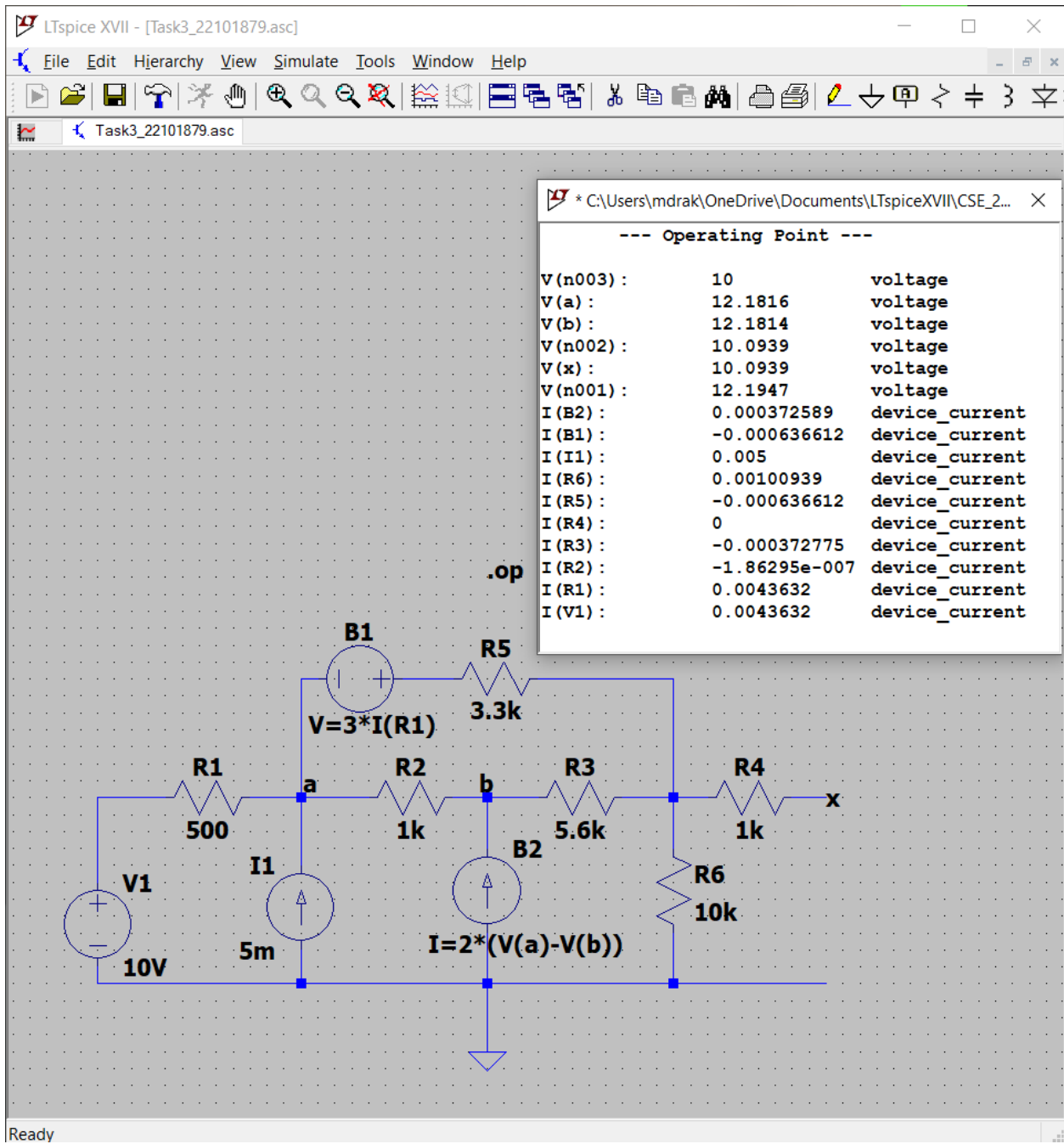


## Task-3.2

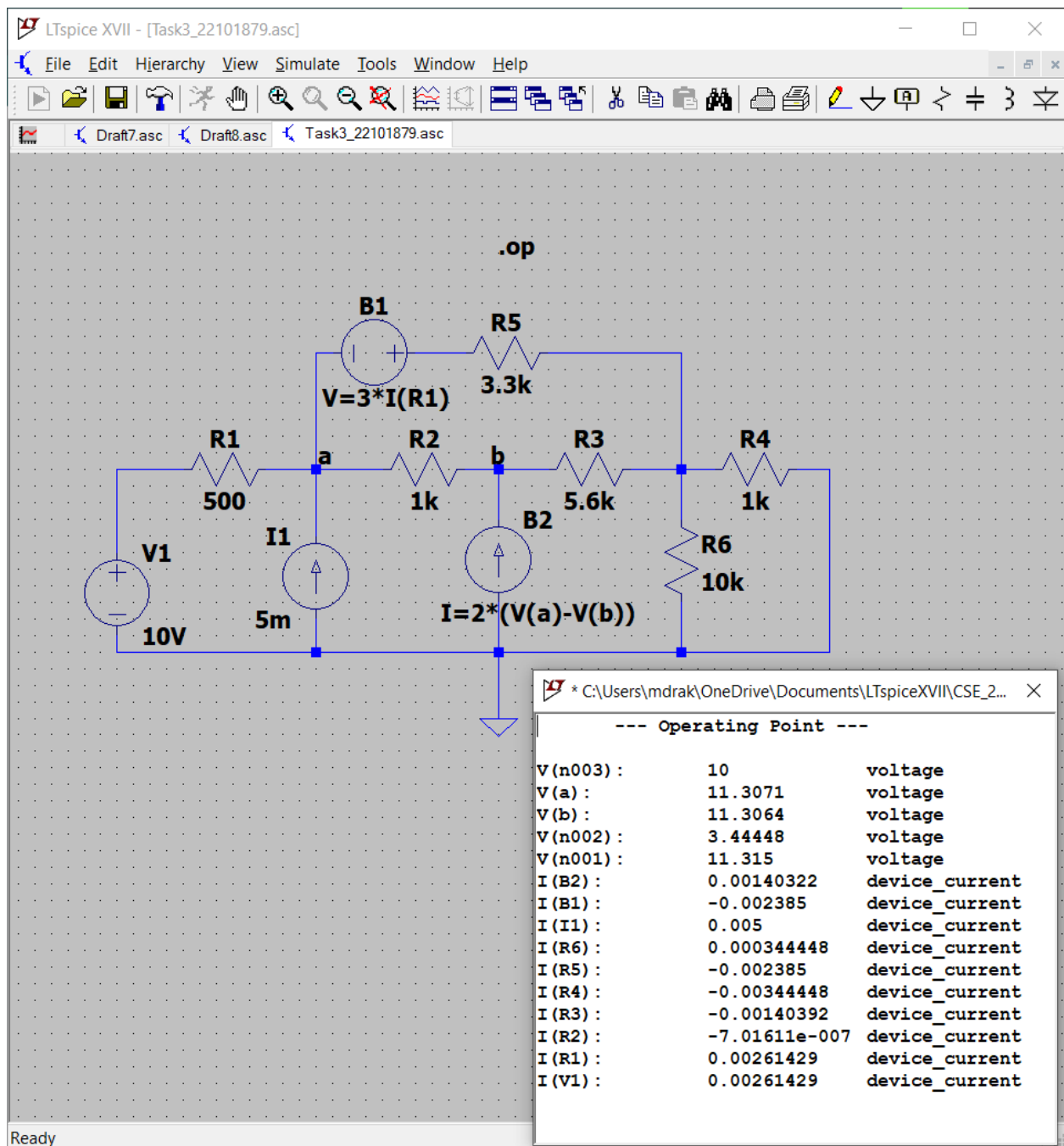

## Task-4

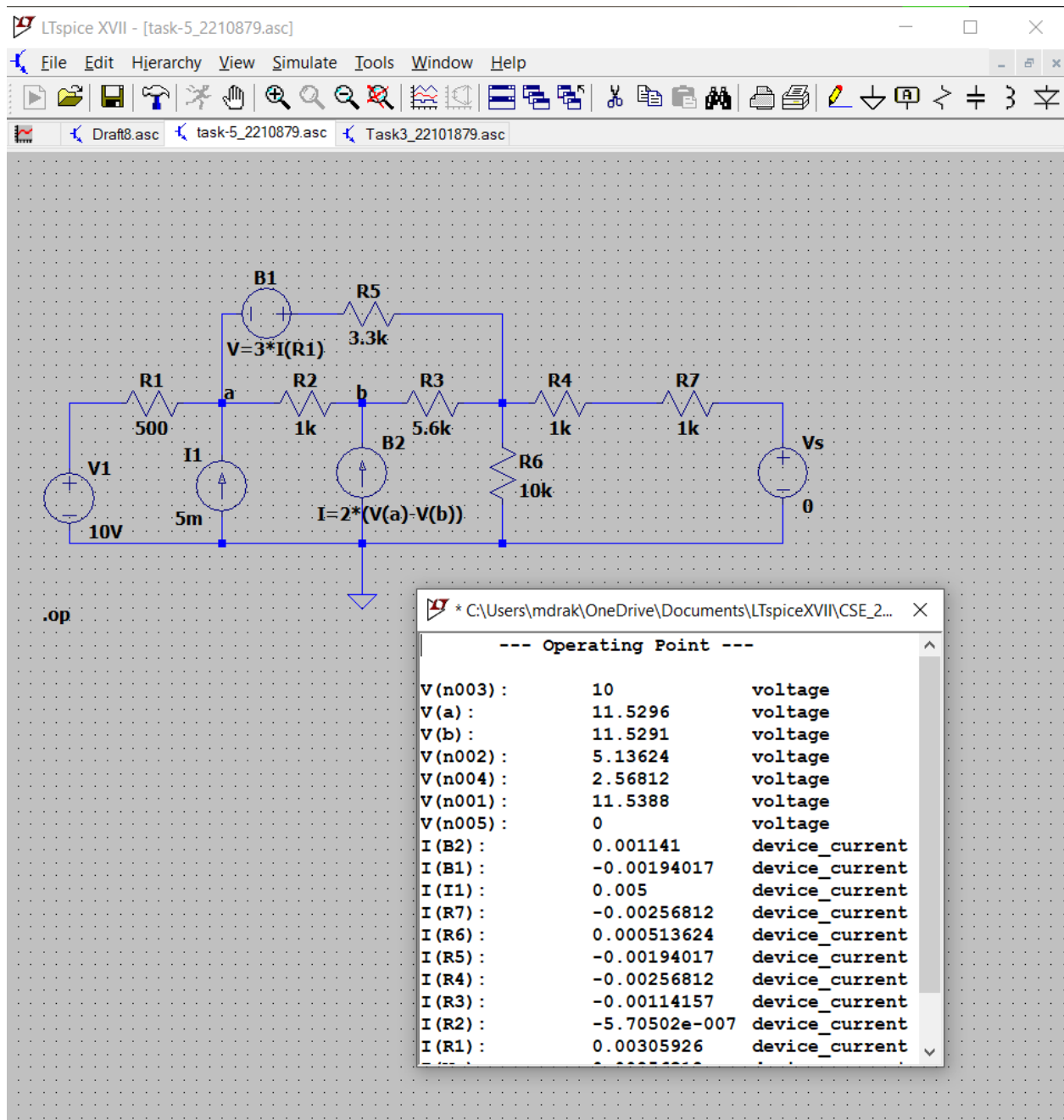


## Task-6:

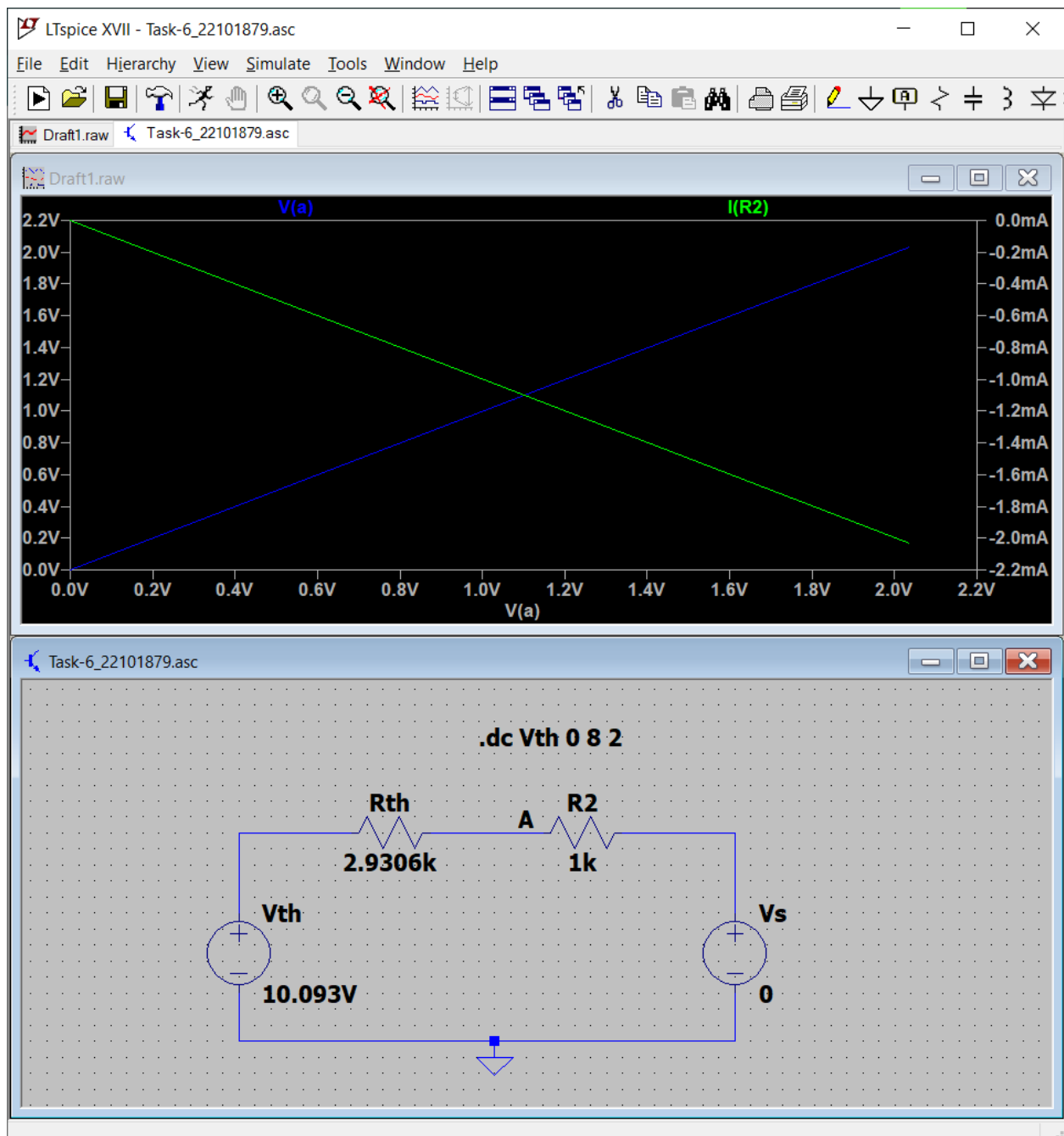

Answer: The given circuit does follow the Thevenin's equivalent circuit, as we know in the Thevenin's theorem the source of voltage  $R_{th}$  is the equivalent resistance of the original circuit as viewed from the output terminals when all sources are off, and  $V_{th}$  is the open-circuit voltage at the original circuit's output terminals. Since the given circuit does the same, so we can say it follows the theorem.

## Task:7

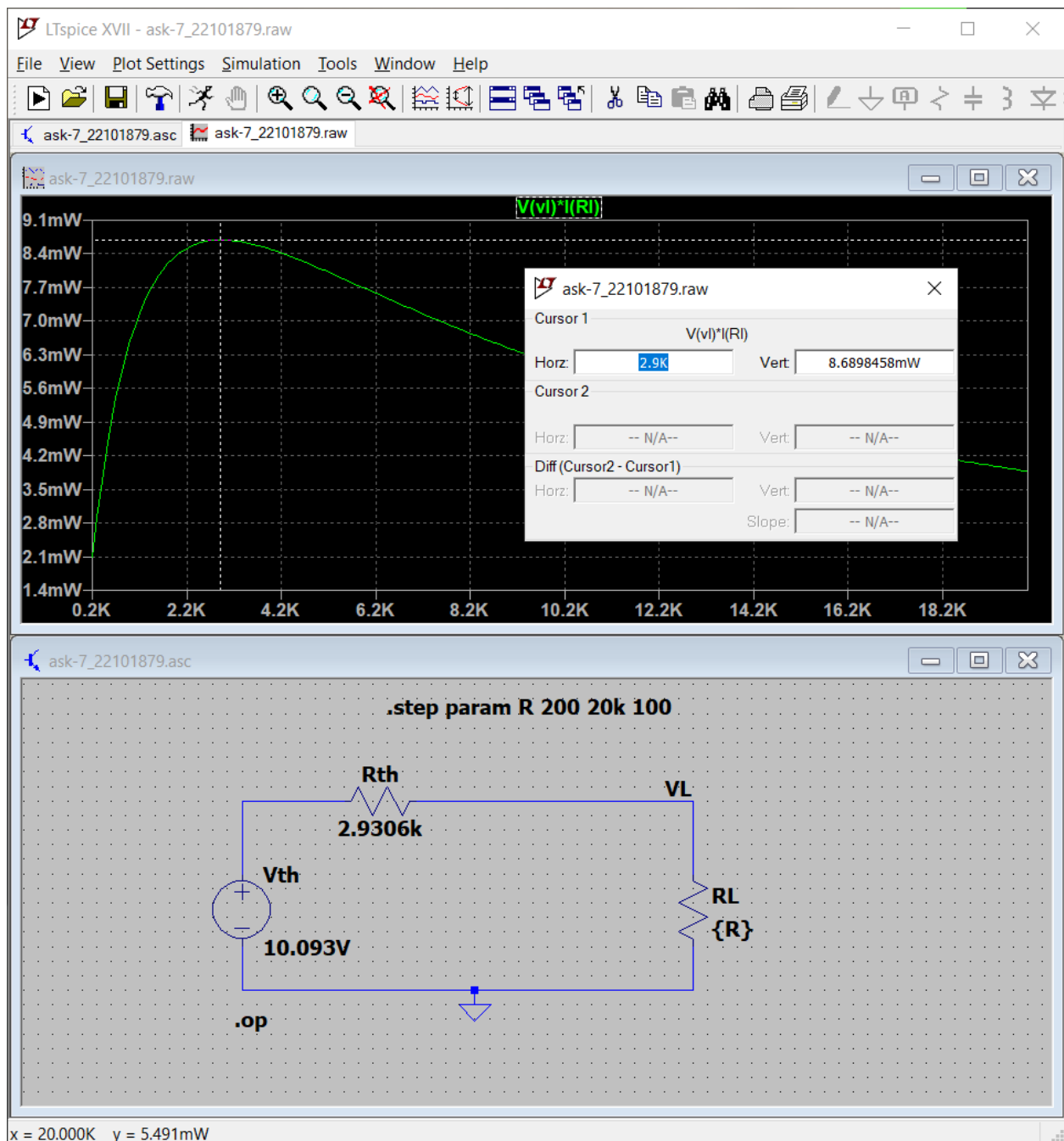

Answer:

From the above plot we can see that the maximum power of  $R_L$  was 8.898458mW at 2.906. So maximum power had been achieved at  $R_{th}$  register. Hence the circuit follows Thevenin's theorem.