



Inspiring Excellence


Department of CSE
CSE250: Circuits and Electronics
Assignment-3
Full Marks: 20
Deadline: 31st August 2023,
11:59 pm

Copying is strictly prohibited. If found plagiarism, he/she will be penalized whole assignment mark. The number inside parentheses at the end of each question indicates the mark of that question.

■ **Question 1 of 1**

[CO3]

[10 marks]

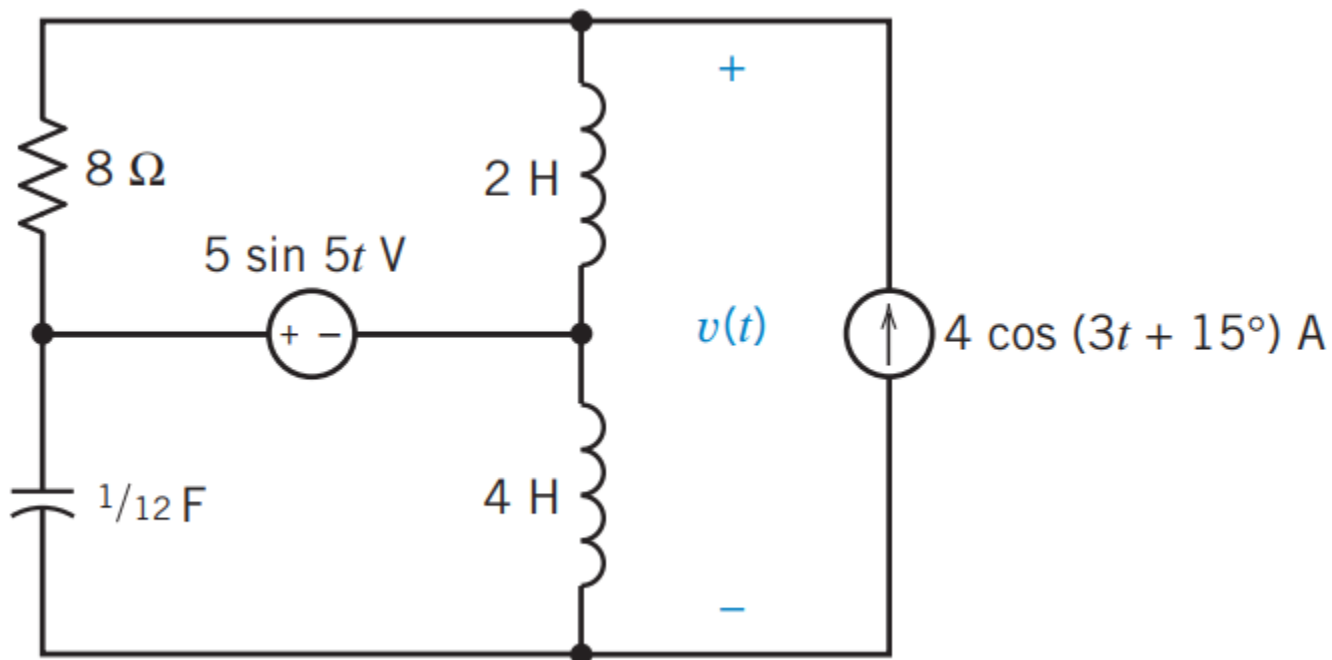

Determine the voltage $v(t)$.